

$$P_{Cu, \text{amb}} = R_{a,\text{tot}} \cdot I_a^2$$

$$R_a + R_b + R_c$$

Generator R_v

$$\eta = \frac{I_m}{U_a \cdot I_a} \cdot 100\%$$

1.7 Vermogenverdeling motor

$$100\%$$

oef 3
oef 5
oef 4

$$\begin{aligned} P_i &= V_a \cdot I_a - R_{\text{rotor}} \cdot I_a^2 \\ &= I_a (V_a - R_{\text{rotor}} \cdot I_a) \\ &= E \cdot I_a \end{aligned}$$

$$\begin{aligned} P_v &= P_{Fe} + (P_R + P_{WS}) \\ &= P_{wrijf} + P_{vent.} \end{aligned}$$

$$\begin{aligned} P_n &= P_{as} = P_{\text{mech.}} = P_i - P_v \\ &= P_{\text{kemplaat}} \end{aligned}$$

$$E < U_a$$

L. Butaye – academiejaar 2024-2025

<<

\longleftrightarrow

P_{motor}

$$P = M \cdot \omega$$

$$M_i = \frac{P_i}{\omega}$$

$$M_v = \frac{P_v}{\omega}$$

$$M_n = \frac{P_n}{\omega}$$


$$M_i = M_v + M_n$$

$\text{eff } \frac{1}{e}$

1.8 Vermogenverdeling dynamo

$$P_t = \rightsquigarrow P_{\text{mech}} - P_{\text{verplaats}} \quad \text{100%}$$

$$P_v = P_{F2}$$

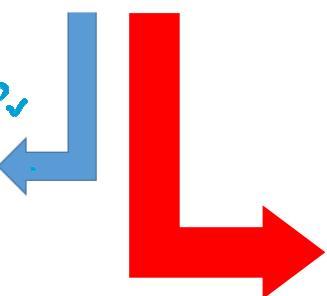

$$P_i = E \cdot I_a$$

$$P_{\text{Cu}} = R_{\text{aator}} I_a^2$$


$$\eta = \frac{V_a I_a}{P_t} \cdot 100\%$$

$$\begin{aligned} P_i &= P_{\text{Cu}} \\ \text{elctr. } P_i &= E \cdot I_a - R_{\text{aator}} \cdot I_a^2 \\ &= V_a \cdot I_a \end{aligned}$$

$$\begin{aligned} P &= M \cdot \omega \rightarrow M_{\text{mech}} = \frac{P_{\text{mech}}}{\omega} \\ M_v &= \frac{P_v}{\omega} \\ M_i &= \frac{P_i}{\omega} = \frac{E \cdot I_a}{\omega} \\ \hline M_{\text{mech}} &= M_v + M_i \end{aligned}$$



$$E > V_a$$

1.9 Kwadrantenwerking


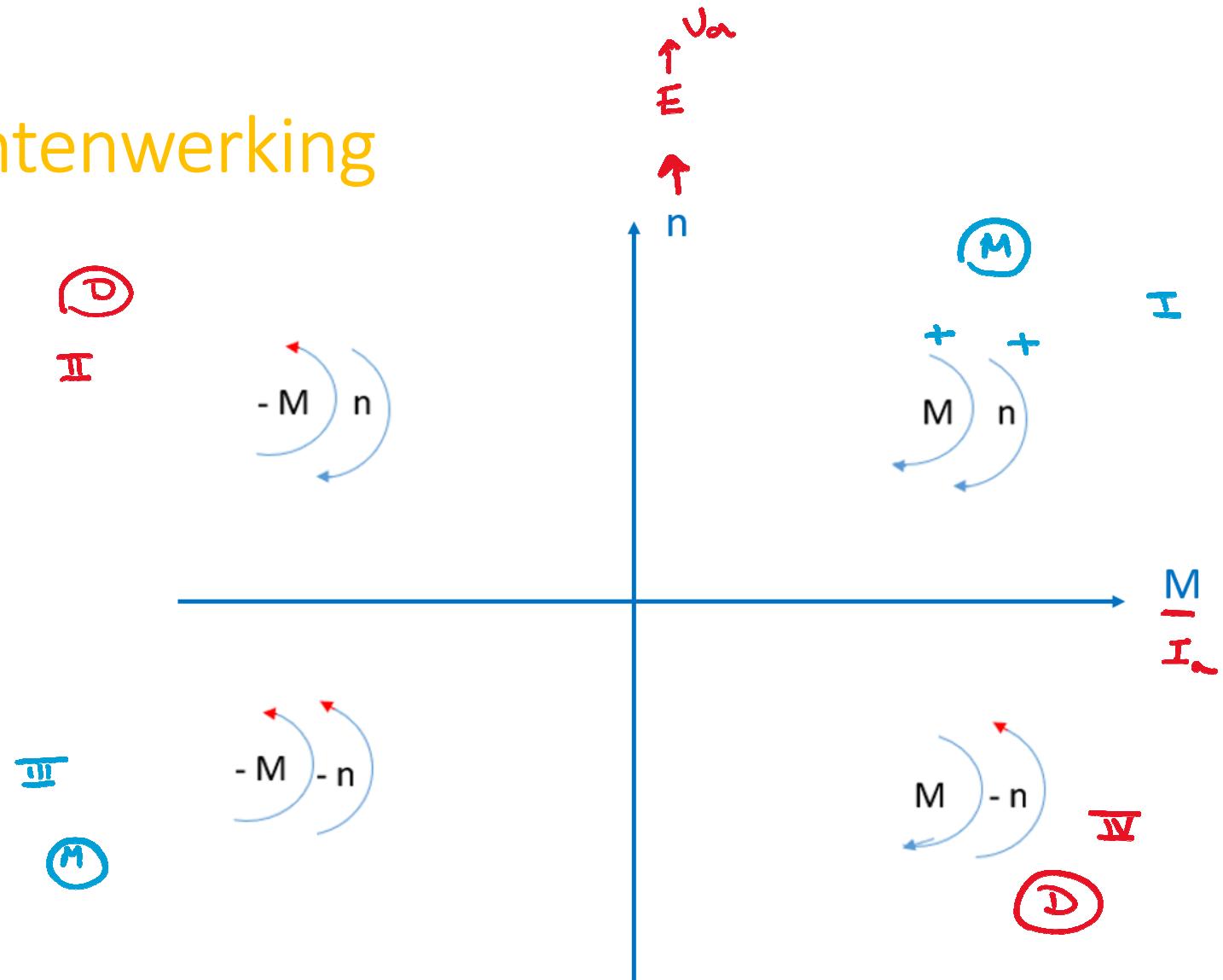


1.9 Kwadrantenwerking

(D)

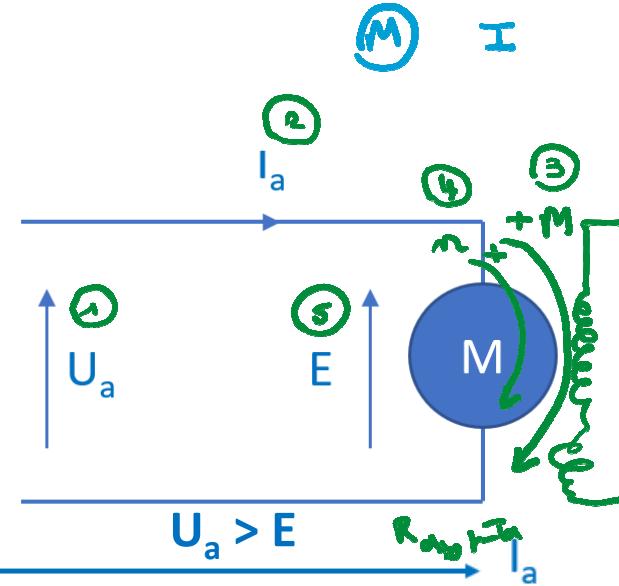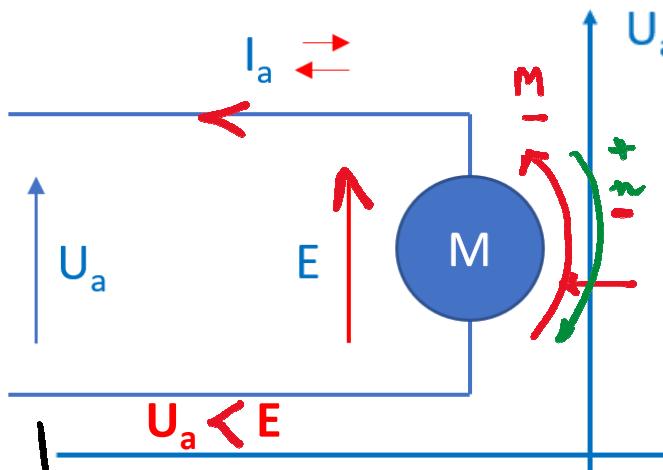


(M)

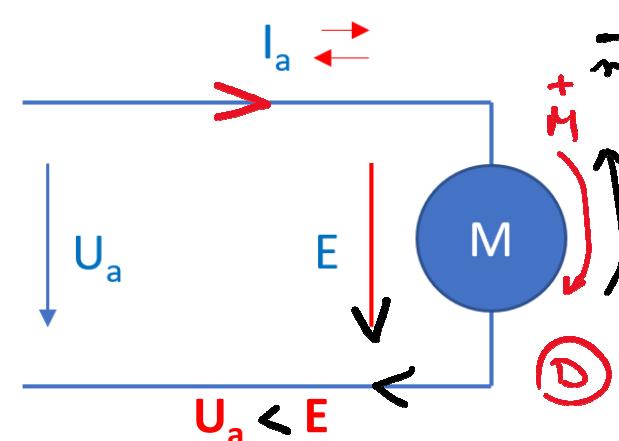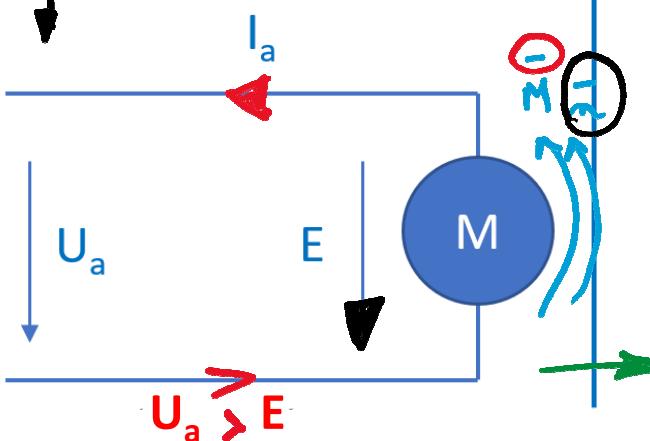

1.10 Onafhankelijk bekraftigde DC-motor

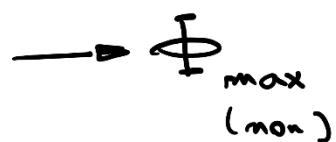1.10.1. EQ.S.


$\left\{ \begin{array}{l} \text{VELD} \\ \text{BEKRACHTIGING} \end{array} \right.$



ANKER

$$R_a + (R_b) + (R_c) = R_{\text{otor}}$$

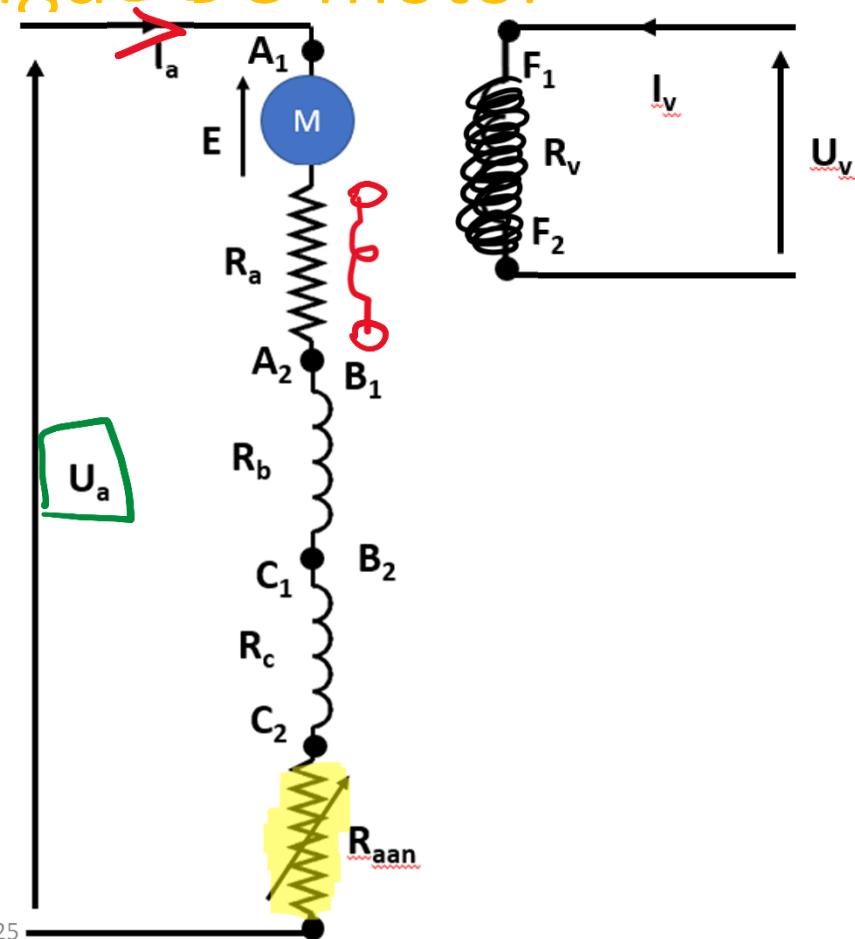START ?? $\rightarrow n=0 \rightarrow E=0 \rightarrow I_{\text{aan}} = \frac{U_a - 0}{R_{\text{otor}}} > >$




1.10 Onafhankelijk bekraftigde DC-motor

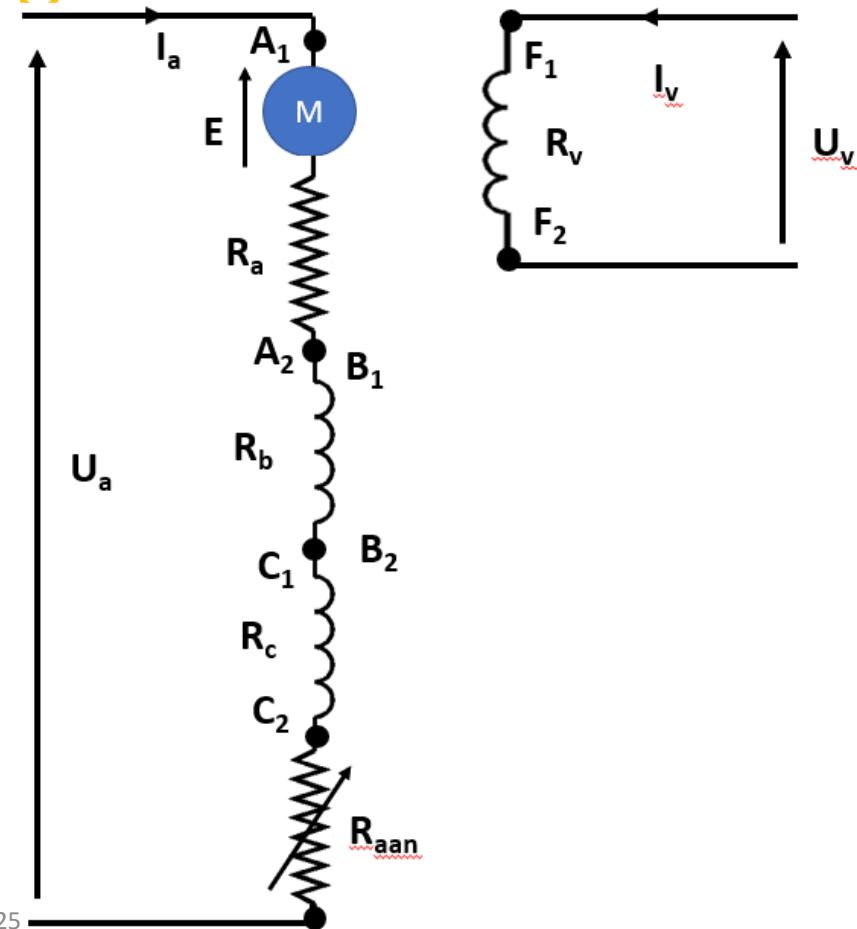1.10.1. EQ.S.

Starten

- $\tau_a < \tau_{veld} \leftarrow L_v > L_a$
- $I_a > I_v$




1.10 Onafhankelijk bekraftigde DC-motor

1.10.2. Veldstroom

$$I_v = \frac{U_v}{R_v}$$

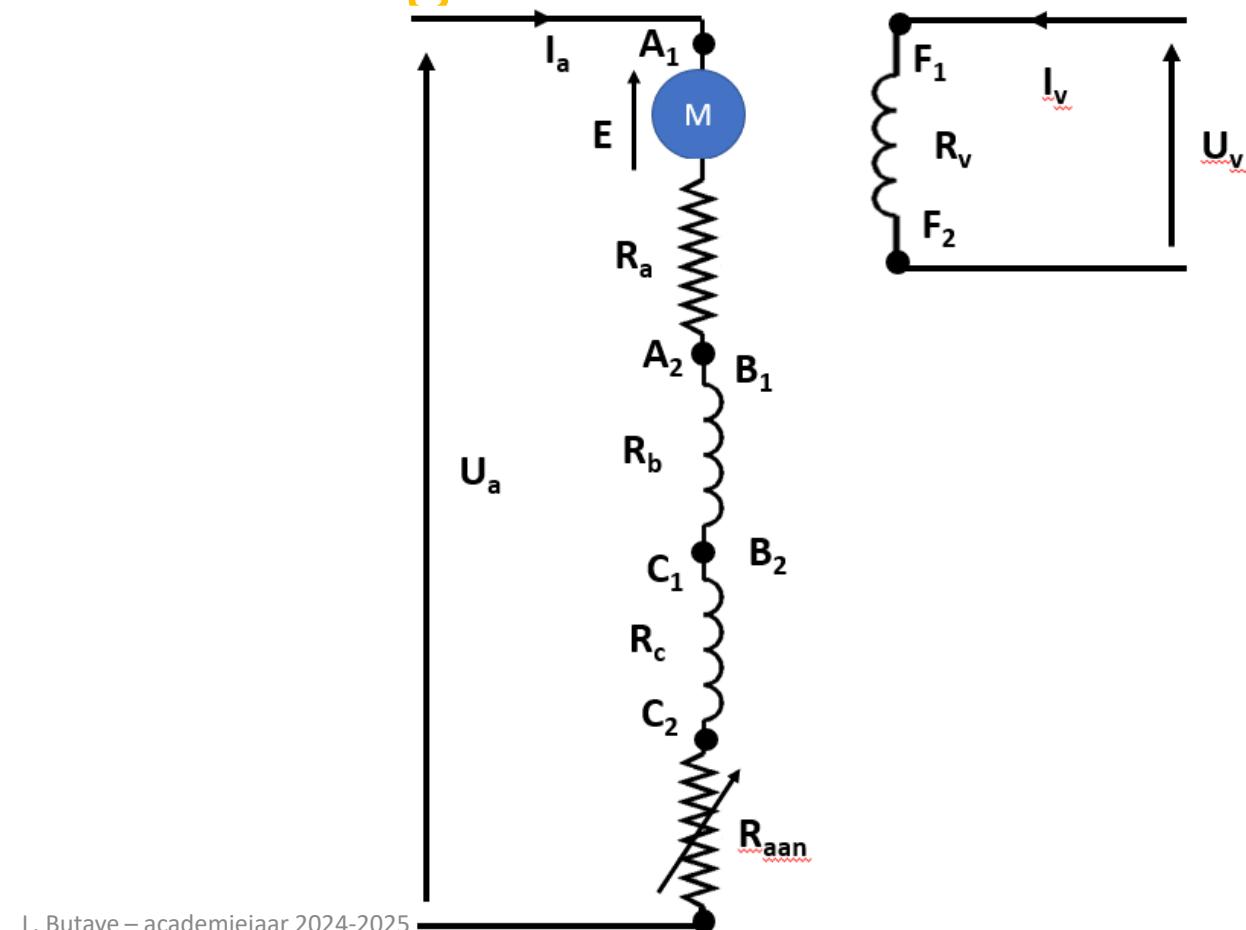1.10.3. Ankerstroom

$$I_a = \frac{U_a - E}{R_{\text{ator}}}$$



1.10 Onafhankelijk bekraftigde DC-motor


1.10.4. Koppel $M_i = f(I_a)$

$$M_i = k_2 \Phi I_a$$


$$M_i \sim I_a \rightarrow \text{RECHTE}$$

(+, +)
↓

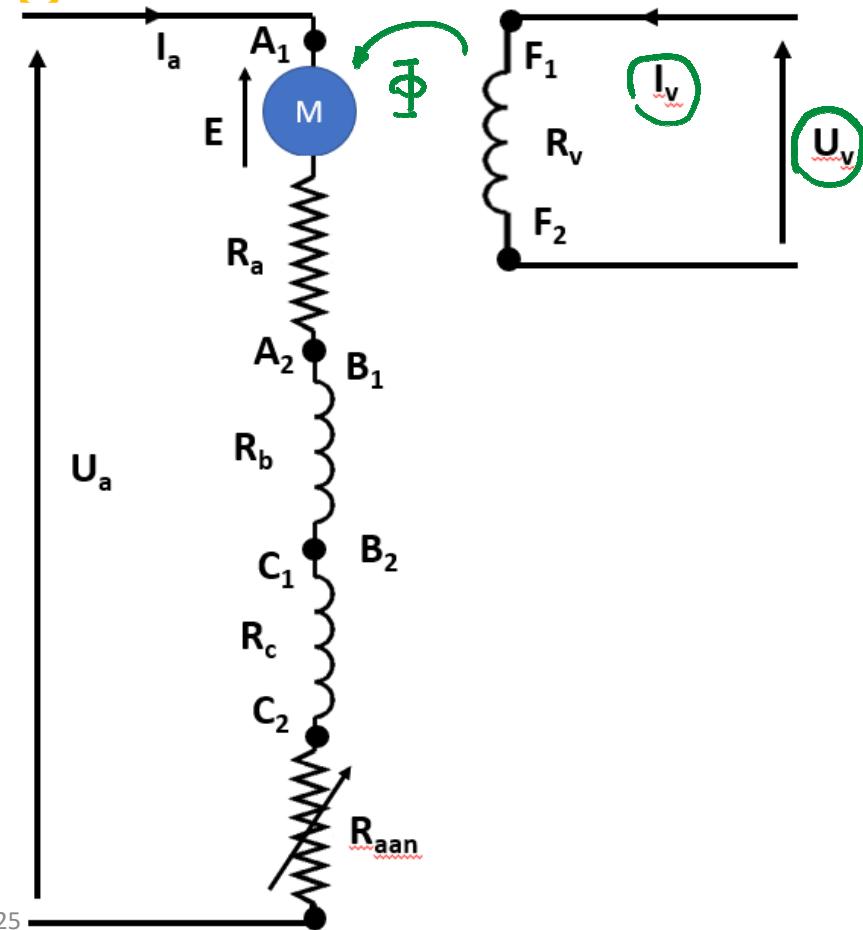
$$I_a = 0 \rightarrow \Phi = 0 \rightarrow M_i = 0$$



1.10 Onafhankelijk bekraftigde DC-motor

1.10.4. Koppel $M_i = f(I_a)$

VGL ASM

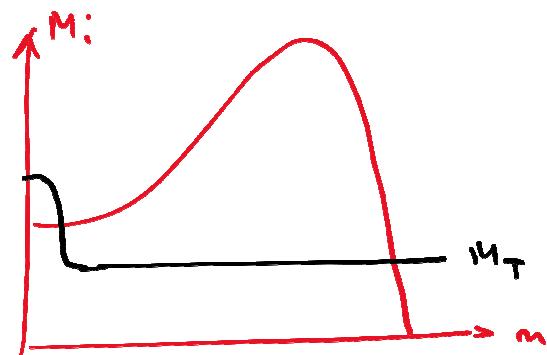

→ DC

$$M_i = k_2 + I_a$$

$$1.5 M_{i_m} \leftarrow 1.5 I_{a_m}$$

LOSBREEKKOPPEL

1.10 Onafhankelijk bekraftigde DC-motor

1.10.4. Koppel $M_i = f(I_a)$

$$\phi = c^{\text{te}} !!$$

① $M_T = M_i$


{

nominaal $\rightarrow M_{i\text{m}}$ $\rightarrow I_{a\text{m}}$

② $M_T \downarrow \rightarrow I_a \downarrow$

③ $M_T \sim \frac{M_{i\text{m}}}{I_a}$

④ NULL AST

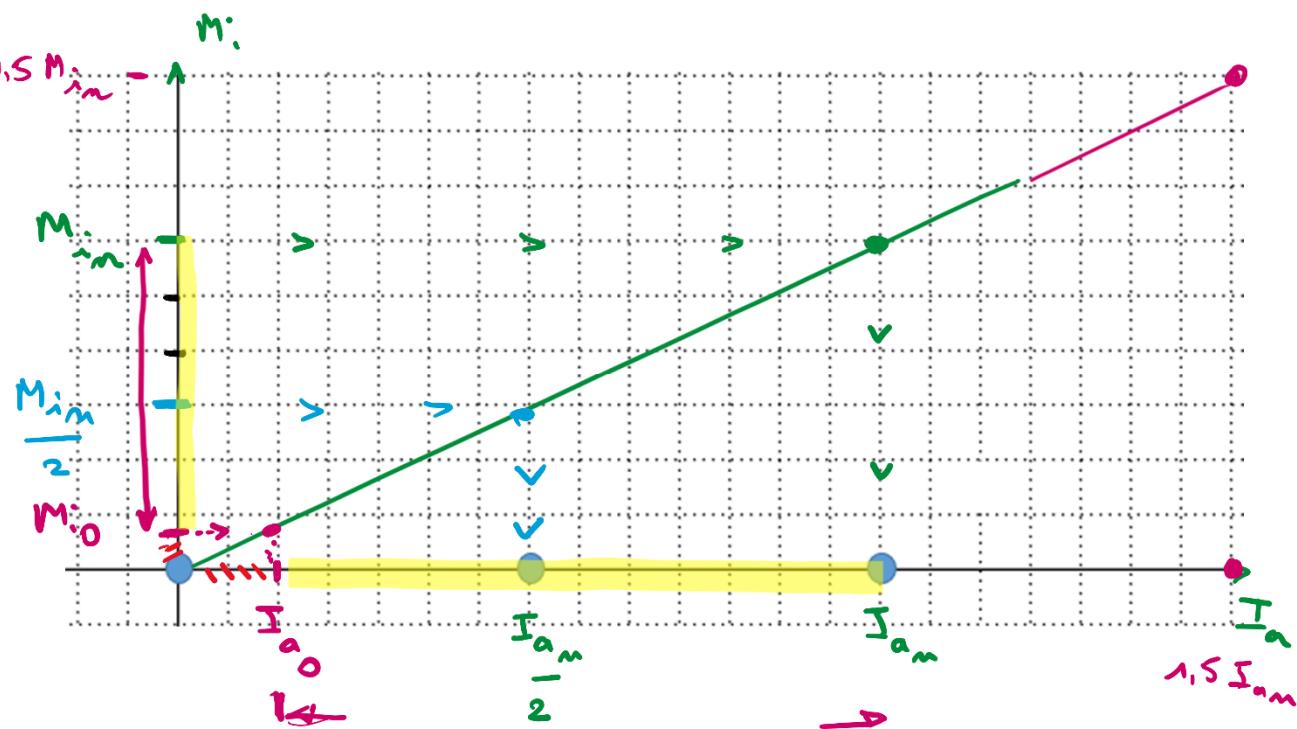

1.10 Onafhankelijk bekraftigde DC-motor

1.10.5. Toerental $n = f(I_a)$


$$n ? \rightarrow E = k_s n \cdot \phi$$

$$\phi = k_e$$

$$\Rightarrow n = \frac{E}{k_s \phi}$$

$$= U_a - R_{\text{ator}} \cdot I_a$$
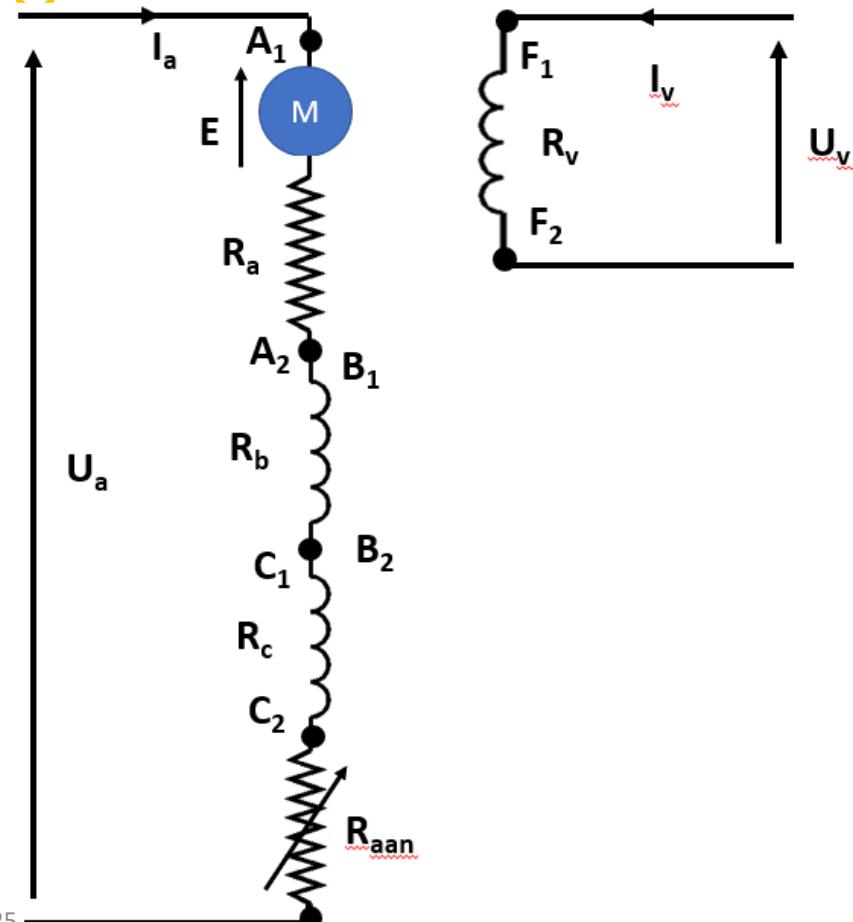
$$\Rightarrow n = \frac{U_a}{k_s \phi} - \frac{R_{\text{ator}}}{k_s \phi} \cdot I_a$$



1.10 Onafhankelijk bekraftigde DC-motor

1.10.5. Toerental $n = f(I_a)$

$$n = \frac{V_a}{k_a \phi} - \frac{R_{\text{motor}}}{k_a \phi} \cdot I_a$$

$\downarrow \quad \quad \quad \downarrow$

$$y = b - a \cdot x$$

$\downarrow \quad \quad \quad \downarrow$

SNYPT NEG RICO

$y_{-\infty}$

1.10 Onafhankelijk

1.10.5. Toerental $n = f(I_a)$

① $M_T \downarrow$


$$M_i \uparrow \quad k_e \neq I_a \quad \boxed{\downarrow}$$

Rotor $I_a \downarrow$

$E \uparrow$

$m \uparrow$

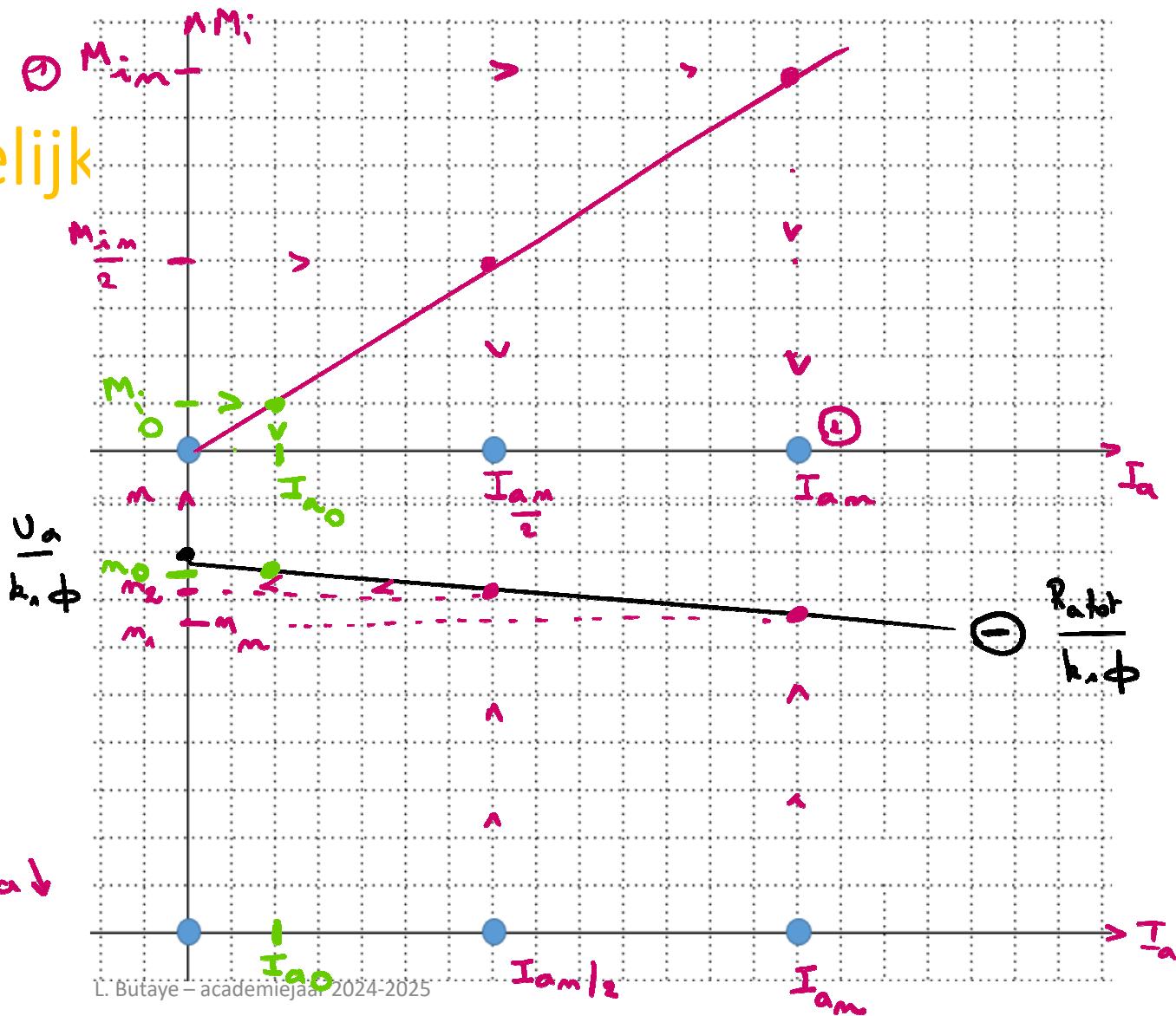② $M_T \downarrow \rightarrow m \uparrow \rightarrow E \uparrow \rightarrow I_a \downarrow$



1.10 OB-motor

1.10.6. Koppel $n = f(M_i)$


$$M = \frac{U_a}{k_1 \phi} - \frac{R_{motor}}{k_1 \phi} \cdot I_a$$

$$M_i = k_2 \phi I_a$$

$$I_a = \frac{M_i}{k_2 \phi}$$

$$n = \frac{U_a}{k_1 \phi} - \frac{R_{motor}}{k_1 \phi} \cdot \frac{1}{k_2 \phi} \cdot M_i$$


Rico

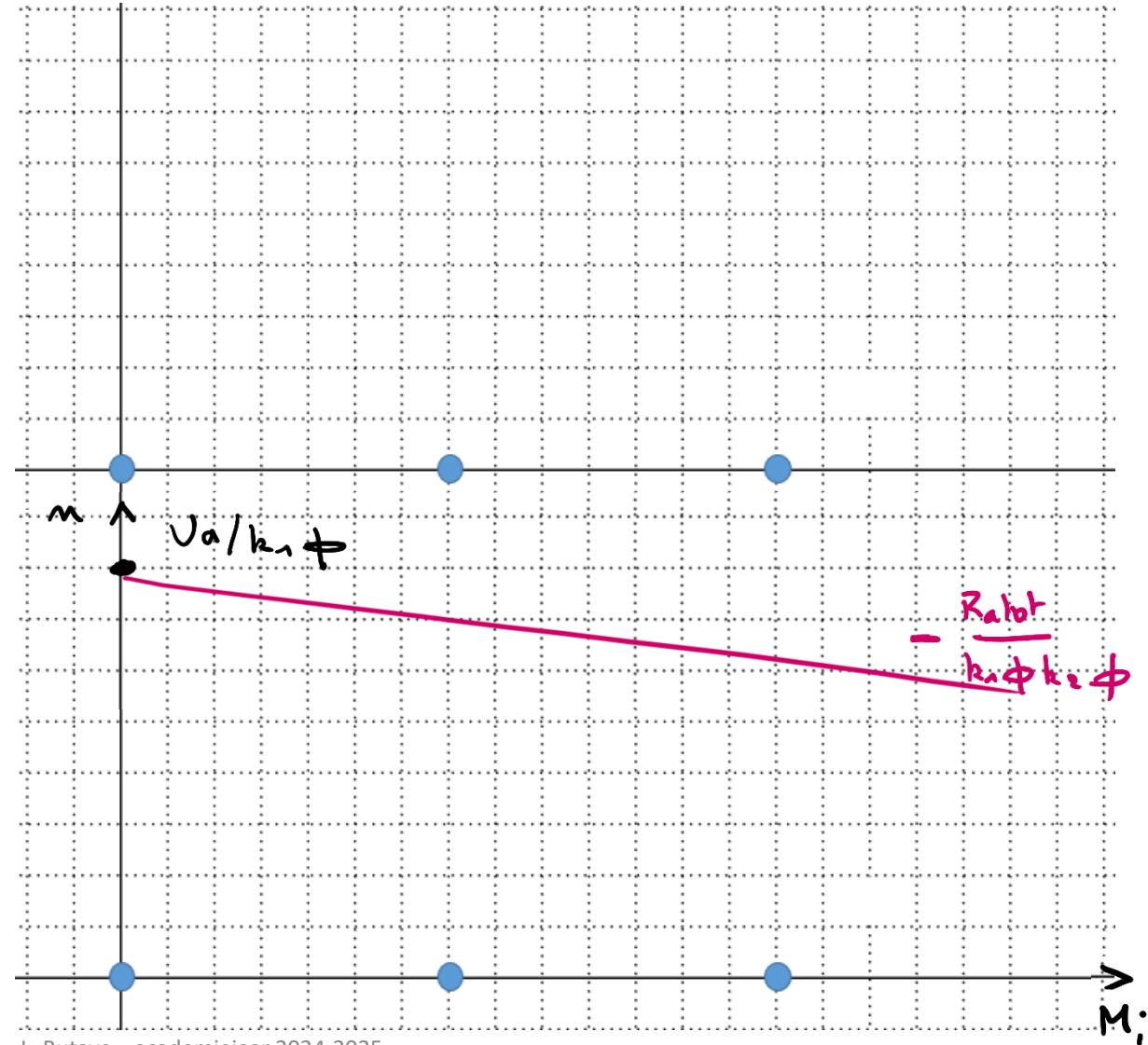

1.11 Shunt (DC-)motor

1.11.1. EQ.S.

VELD \parallel anker

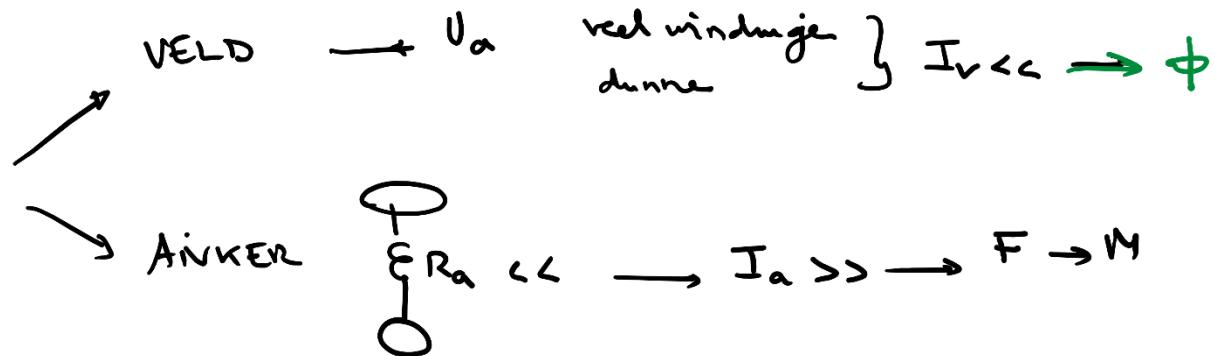


OEF SHUNT-MOTOR neemt ee stroom van 102A

$$I_{tot} = 102A$$

$$I_v = \frac{U_a}{R_v} = 2A$$


$$\left. \begin{array}{l} I_a = 100A \\ \rightarrow E \\ \rightarrow n \end{array} \right\}$$

L. Butaye – academiejaar 2024-2025

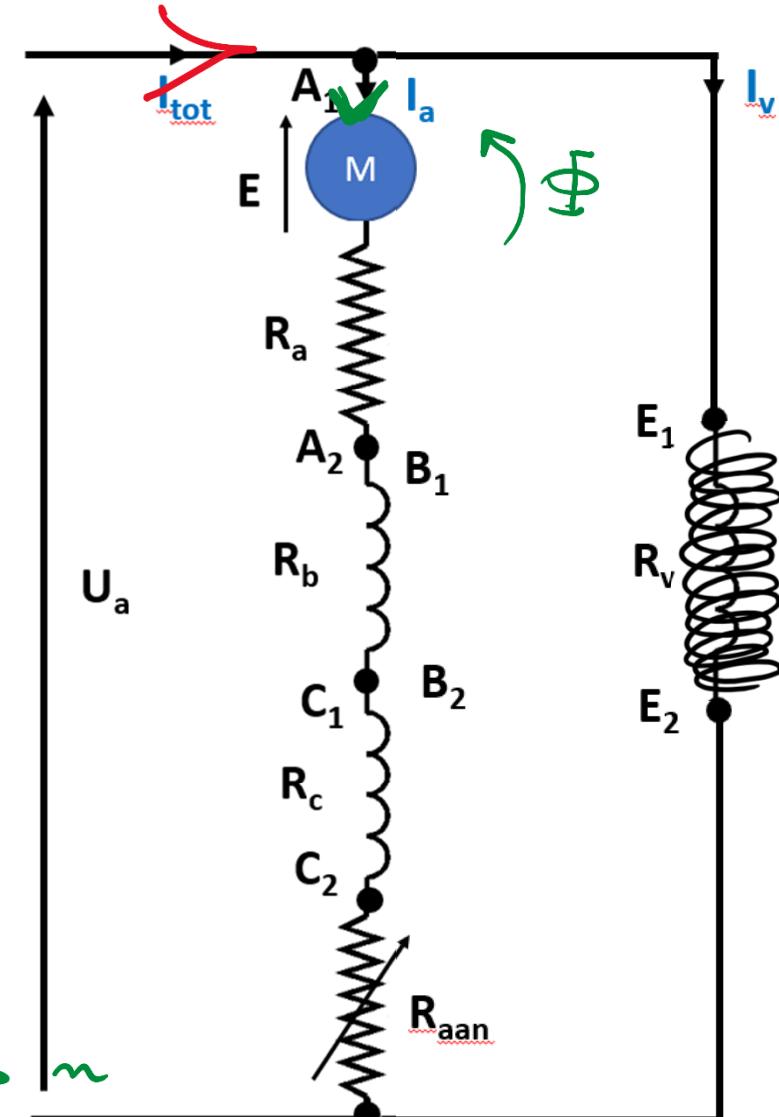

1.11 Shunt (DC-)motor

1.11.1. EQ.S.

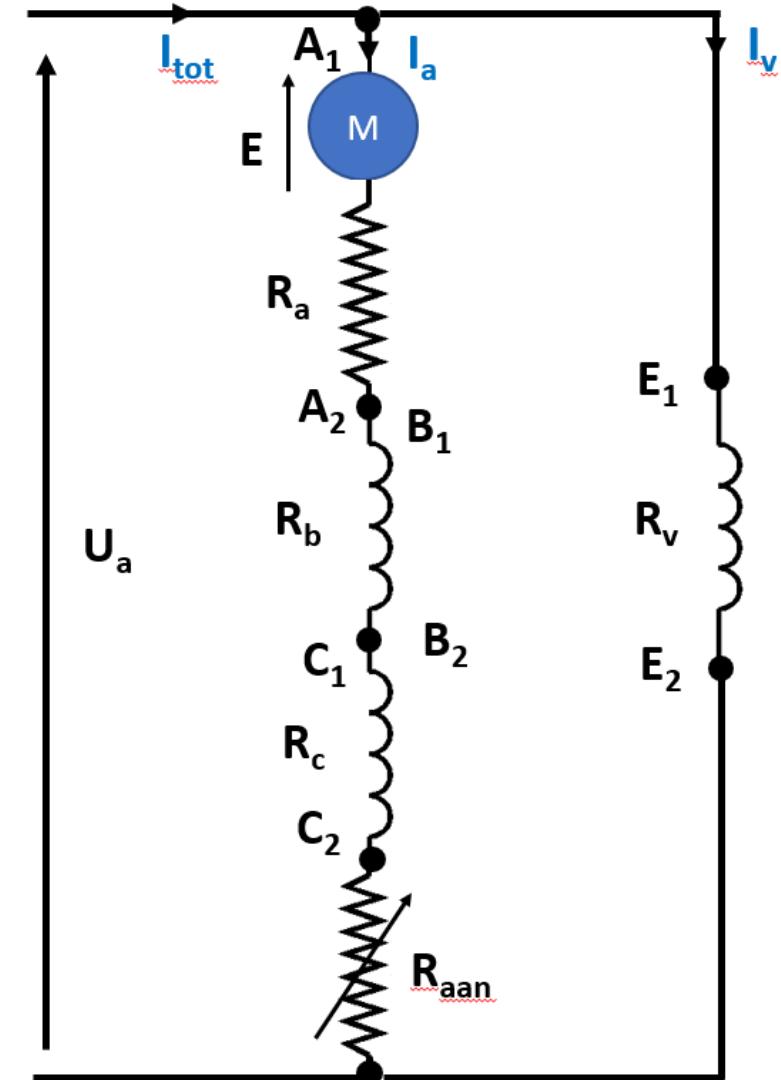

1.12 Serie (DC-)motor

1.12.1. EQ.S.

① VELD in serie ANKER



VELDWIKK




D₁ D₂

② I_a >> \rightarrow weinig verandering } $\rightarrow R_v \ll$



LIN voor VERZ

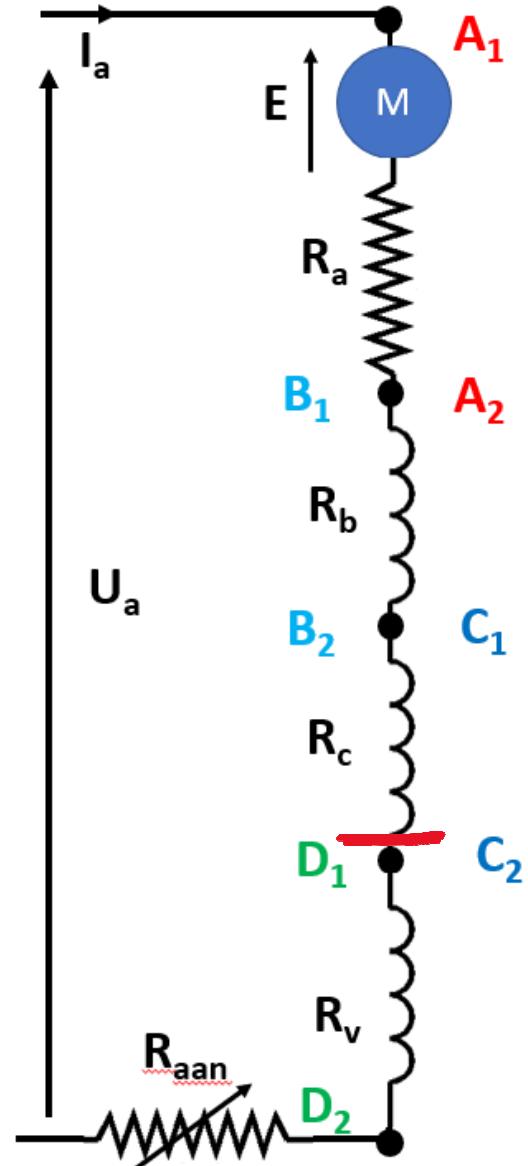③ $\phi \leftarrow I_a$ VERZ $\phi \approx c.k.$



1.12 Serie (DC-)motor

1.12.2. Koppel $M_i = f(I_a)$

$$M_i = k_2 \propto I_a$$


↓
x

voor verz $\phi \sim I_a \Rightarrow \phi = \underline{k'} I_a$

- $M_i = k_2' I_a^2$ kwadr.

- vanaf verz $\phi = c t \rightarrow M_i = k_2'' I_a$

L. Butaye – academiejaar 2024-2025

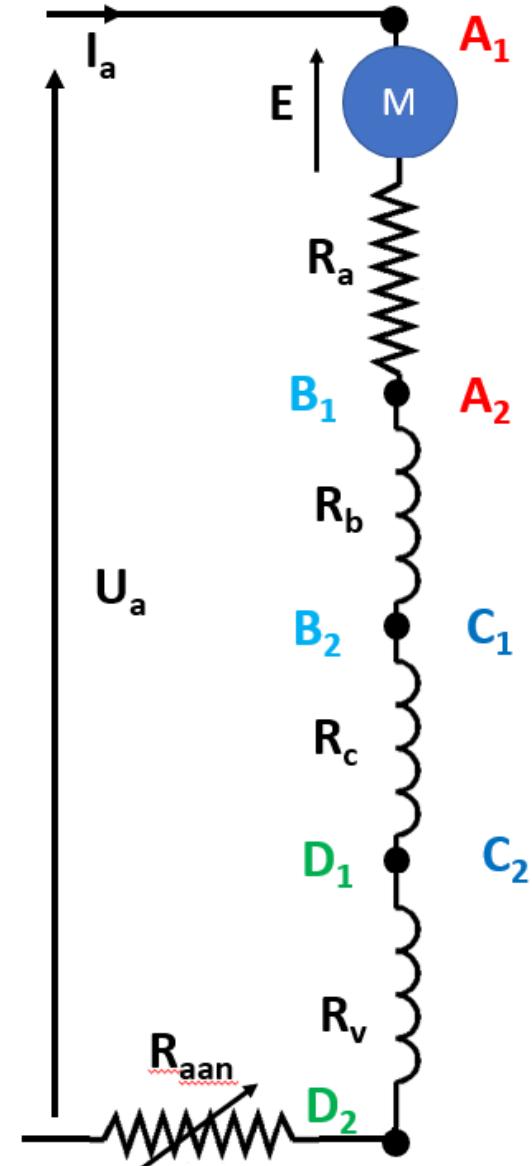


1.12 Serie (DC-)motor

1.12.2. Koppel $M_i = f(I_a)$

1.12 Serie (DC-)motor

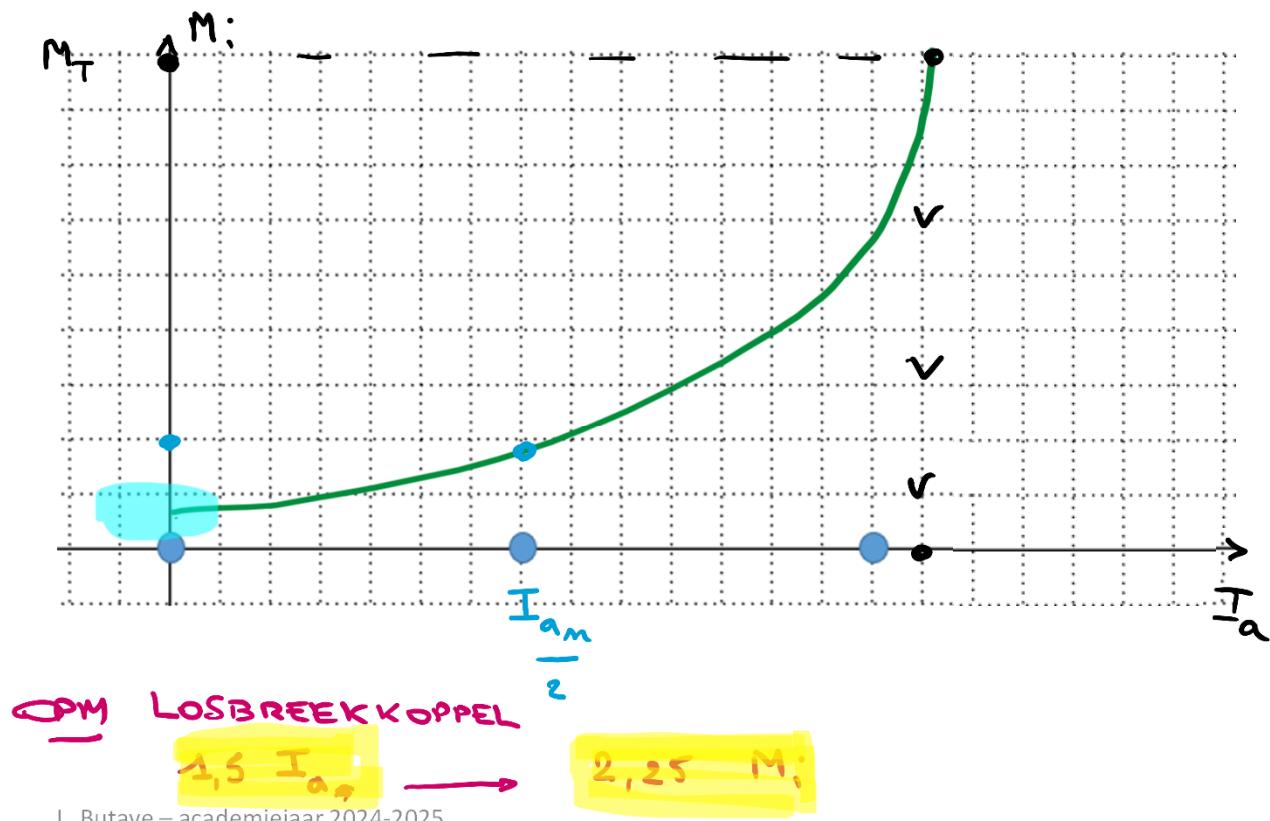1.12.2. Koppel $M_i = f(I_a)$

- $\frac{I_{a_m}}{2}$
- $M_T \uparrow$
- $M_n \uparrow$
- $k_2 \propto \frac{I_a}{T_a}$
- $I_a \uparrow \rightarrow D_1 \dots D_2$
- $\phi \uparrow$
- $M_i \uparrow$



1.12 Serie (DC-)motor

1.12.3. Toerental $n = f(I_a)$

$$E = R_a \cdot n \propto \phi$$

$$n = \frac{U_a - R_{\text{ator}} \cdot I_a}{k_a \circlearrowleft \phi}$$


$\phi \sim I_a$ voor verz.

$$n = \frac{U_a - R_{\text{ator}} \cdot I_a}{k'_1 \circlearrowleft I_a}$$

$$\begin{array}{l} I_a \neq 0 \\ I_a \neq \infty \end{array}$$

$$n = \frac{U_a}{k'_1 I_a} - \frac{R_{\text{ator}} \cdot I_a}{k'_1 I_a} \equiv \frac{U_a}{k'_1 I_a} - \frac{R_{\text{ator}}}{k'_1}$$

L. Butaye – academiejaar 2024-2025

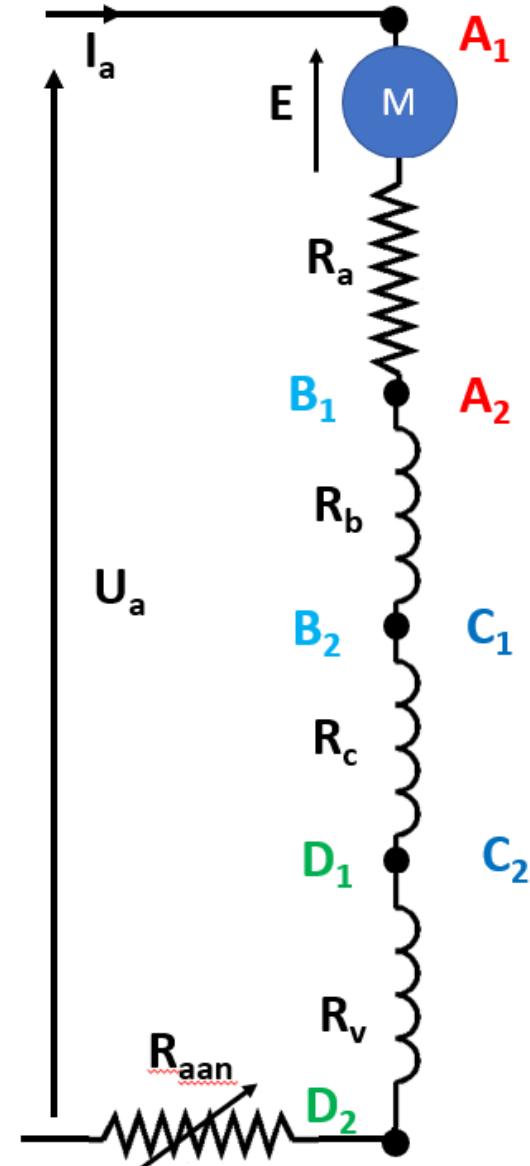

1.12 Serie (DC-)motor

1.12.3. Toerental $n = f(I_a)$

$$n = \frac{V_a}{k'_1 \cdot I_a} - \frac{R_{motor}}{k'_1}$$

$$y = \frac{a'}{x} - b'$$


Hyperbool \longrightarrow 

1.12 Seriemotor

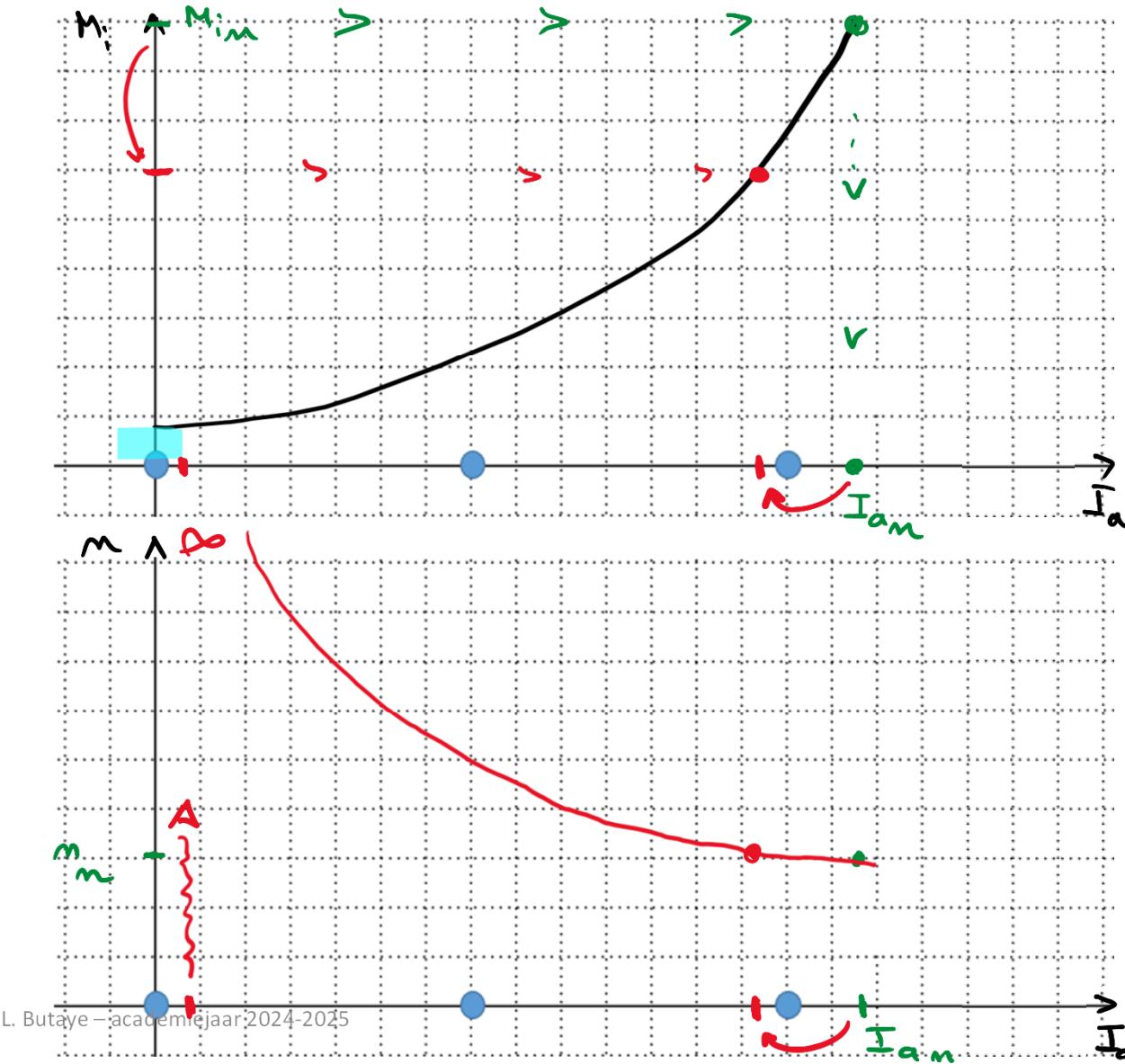1.12.3. Toerental $n = f(I_a)$

$$M_{i_0} ? = k_2 \oplus I_a$$

$I_a = 0$
 $\Phi = 0$
 $E = k_1 \cdot n \cdot \Phi$
eindig



1.13 Toerentalvariatie → OB. MOTOR

1.13.1. Toerental $n = f(M_i)$

1.13 Toerentalvariatie


1.13.2. Parameters toerentalvariatie $n = f(M_i)$

$$E = k_1 \cdot \phi \cdot n$$

$$n = \frac{E}{k_1 \cdot \phi}$$

$$n = \frac{U_a - R_{a,tot} \cdot I_a}{k_1 \cdot \phi}$$

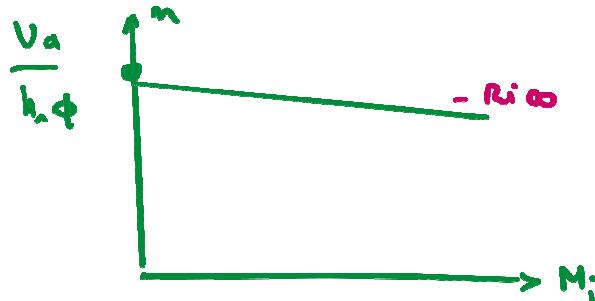en vermits $M_i = k_2 \cdot \phi \cdot I_a$



ONDER VERANDER
X

PARAMETERS

$$n = \frac{U_a}{k_1 \cdot \phi} - \frac{R_{a,tot}}{k_1 \cdot \phi \cdot k_2 \cdot \phi} \cdot M_i$$

$\rightarrow U_a$

$\rightarrow \phi$

$\rightarrow R_{a,tot}$

1.13 Toerentalvariatie

1.13.2. Parameters toerentalvariatie $n = f(M_i)$

$n \downarrow$

1.13.2.1. Variatie in de ankerspanning

$$n = \frac{U_a}{k_1 \cdot \phi} - \frac{R_{a,tot}}{k_1 \cdot \phi \cdot k_2 \cdot \phi} \cdot M_i$$


$\hookrightarrow U_{a,n}$

$\hookrightarrow U_a \leq U_{a,n}$

$\hookrightarrow b \downarrow$

$a =$

$\xrightarrow{\Delta n}$

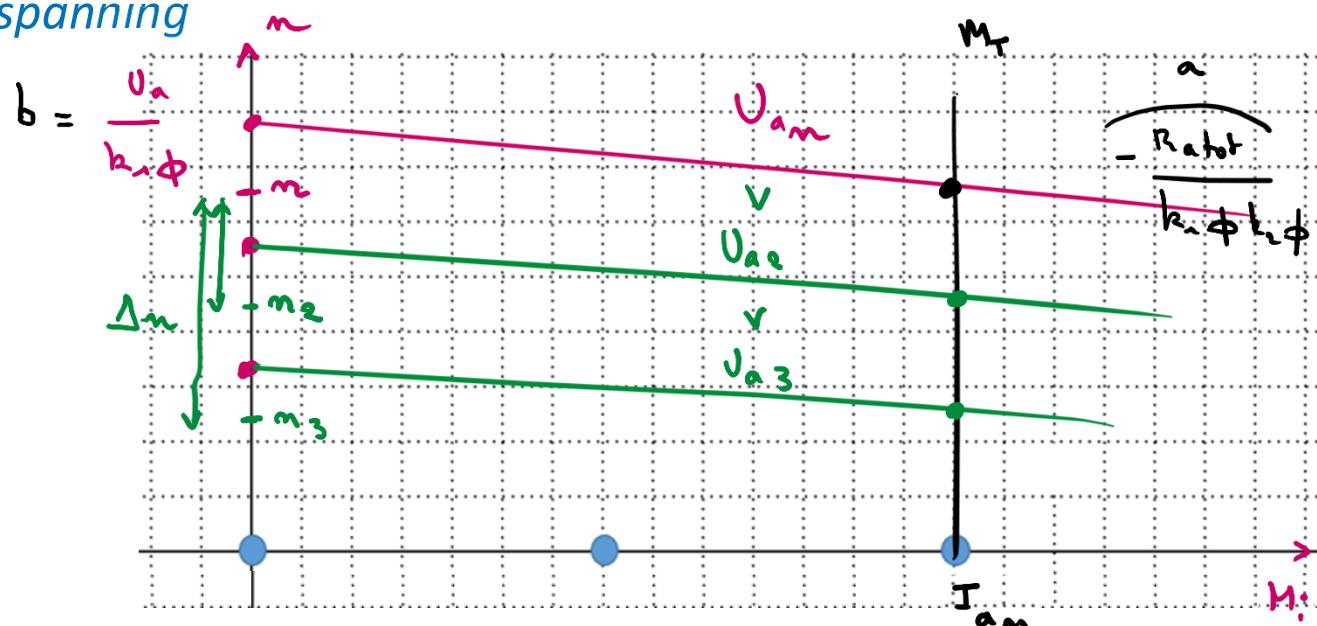

1.13 Toerentalvariatie

$n \uparrow$ $n \rightarrow \infty$?

1.13.2. Parameters toerentalvariatie $n = f(M_i)$

$n \downarrow$ 1.13.2.2. Variatie in het veld
bepaalt


$$n = \frac{U_a}{k_1 \cdot \phi} - \frac{R_{a,tot}}{k_1 \cdot \phi \cdot k_2 \cdot \phi} \cdot M_i$$

ϕ_n
 $\phi < \phi_n$ $\phi > \phi_n$

$b \uparrow$

n_{ico} groter

$n \uparrow$

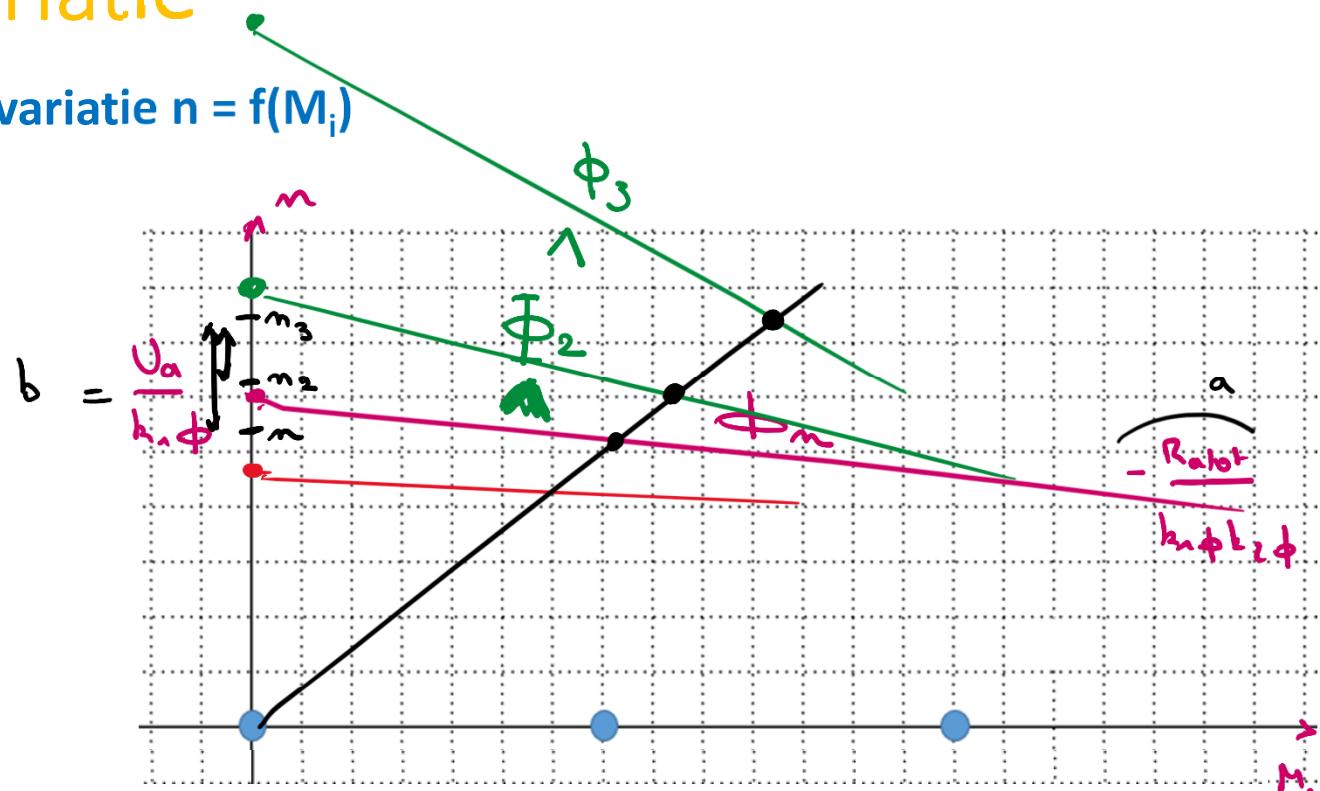

$$M_E = a \cdot n$$

E. Butaye – academiejaar 2024-2025

1.13 Toerentalvariatie

1.13.2. Parameters toerentalvariatie $n = f(M_i)$

1.13.2.3. Variatie in de ankerweerstand

$$n = \frac{U_a}{k_1 \cdot \phi} - \frac{R_{a,tot}}{k_1 \cdot \phi \cdot k_2 \cdot \phi} \cdot M_i$$

↪ $R_{a,tor}$

↪ $R_{a,tor} = R_{ator} + R_{aby}$

↪ $b =$
↪ $R_{icos} \uparrow$

$$M_T = n^2$$

