
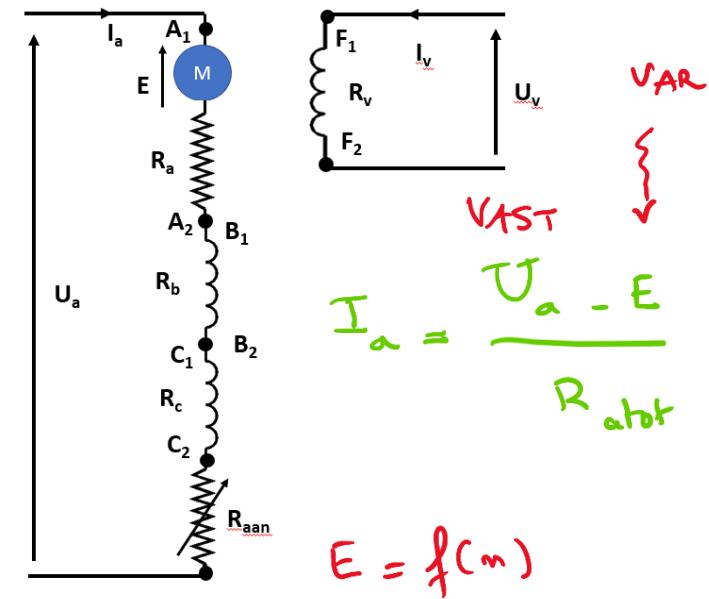


1.14 Aanloop

1.14.1. Aanloopstroom $I_{aan} = f(n)$

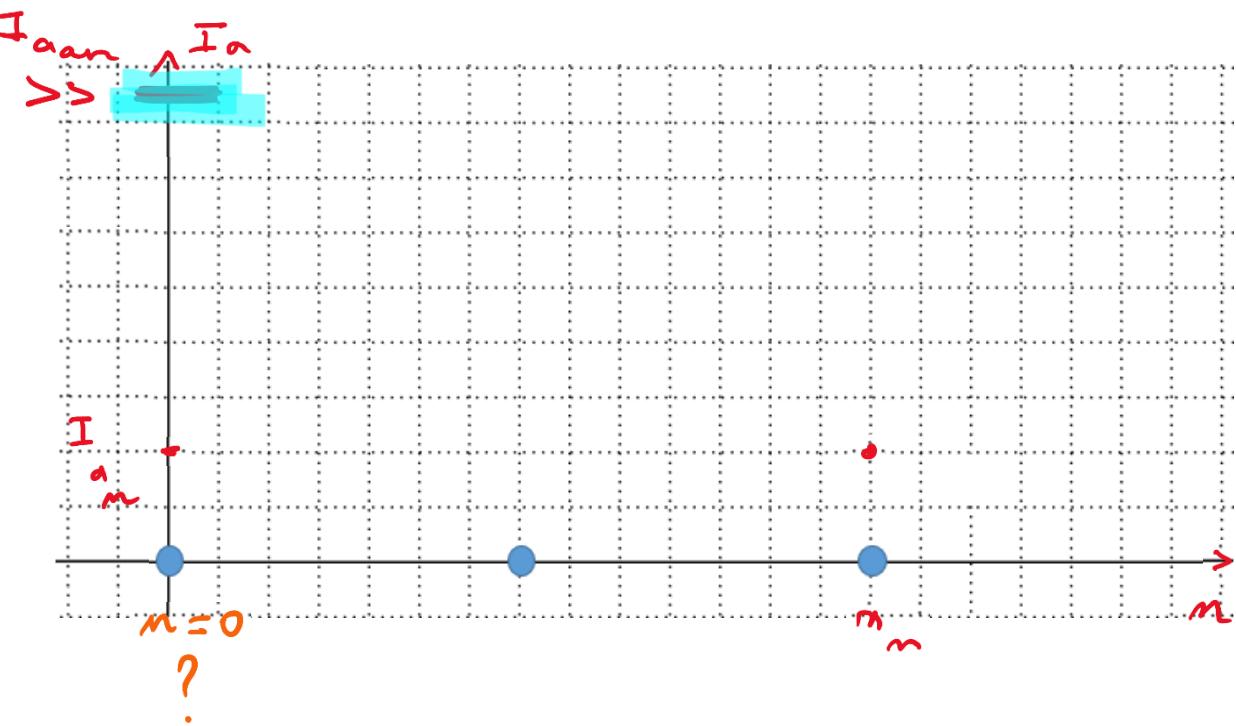


$$I_a = \frac{U_a - E}{R_{atot}}$$




1.14 Aanloop

1.14.1. Aanloopstroom $I_{aan} = f(n)$

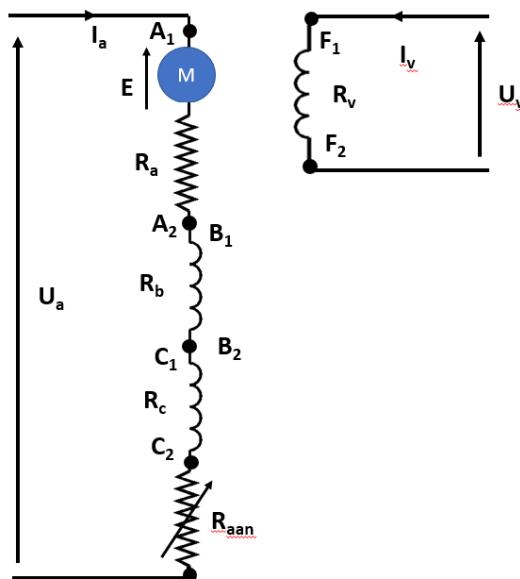

$$n \rightarrow E \gg \rightarrow V_a - E \gg \rightarrow I_a$$
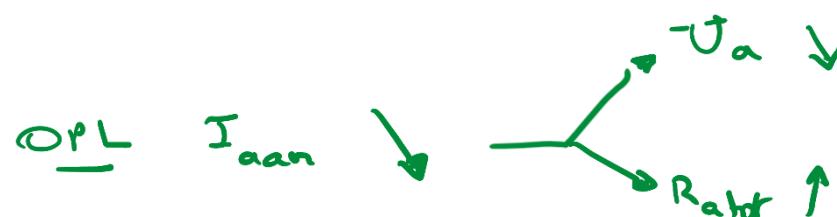
$$n=0 \rightarrow E = k_a n \phi \stackrel{\phi=0}{=} \rightarrow V_a - 0 \rightarrow I_{aan} = \frac{V_a - 0}{R_{ator}}$$



1.14 Aanloop

1.14.2. Aanloopmethoden $n = f(I_{aan})$


1.14.2.1. Variatie in de ankerspanning

$$E = k_a \cdot n \cdot \phi$$

$$n = \frac{E}{k_a \cdot \phi}$$

$$n = \frac{V_a - R_{a\text{tot}} \cdot I_a}{k_a \cdot \phi}$$
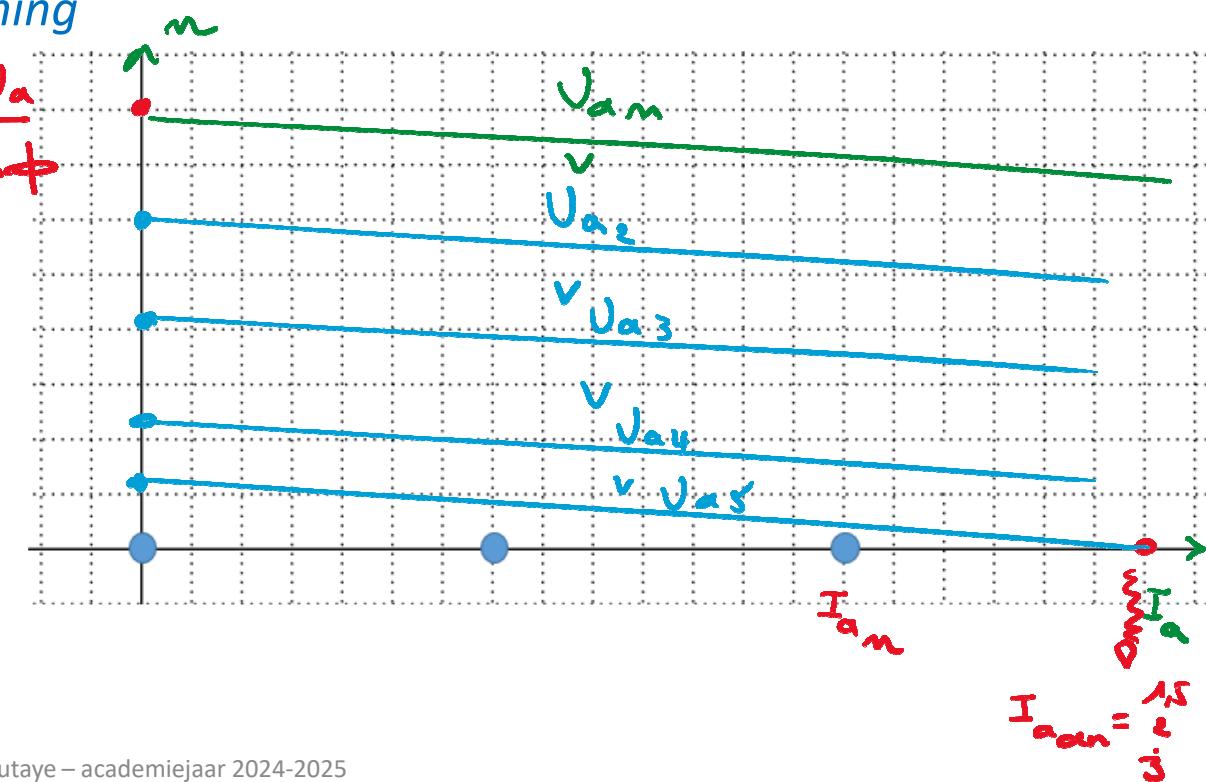
$$n = \frac{V_a}{k_a \cdot \phi} - \frac{R_{a\text{tot}}}{k_a \cdot \phi} \cdot I_a$$




1.14 Aanloop


1.14.2. Aanloopmethoden $n = f(I_{aan})$

1.14.2.2. Variatie in de ankerweerstand

$$n = \frac{U_a}{k_n \phi} - \frac{R_{ator}}{k_n \phi} I_a$$

R_{ator} ↗

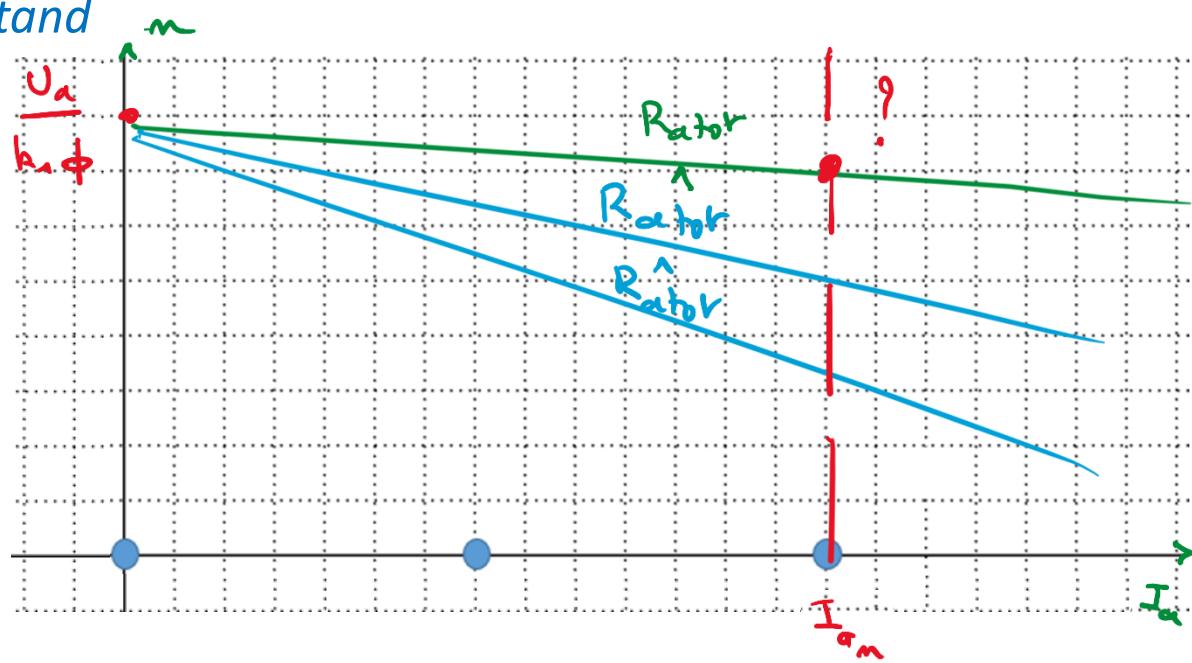

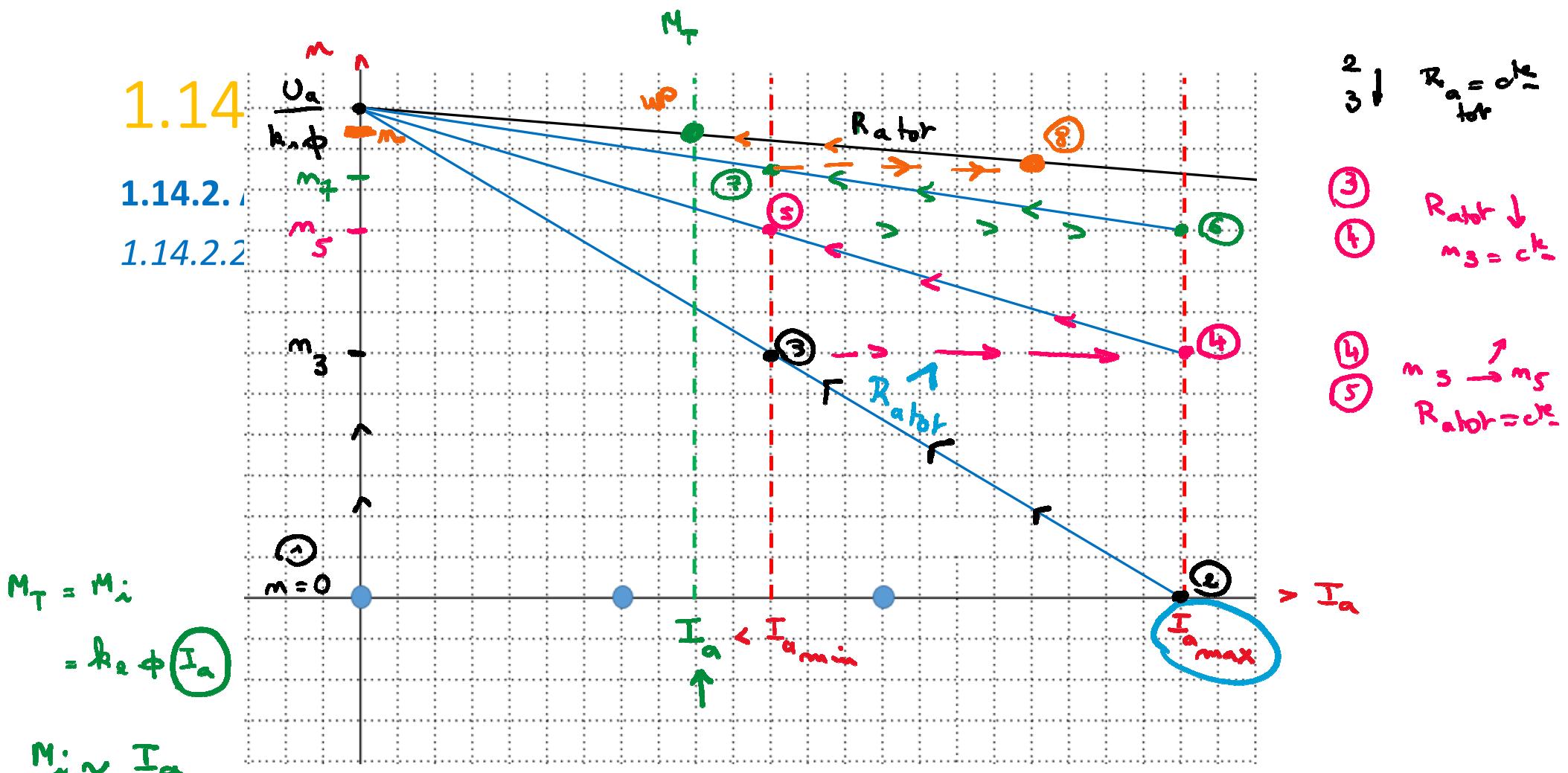

1.14 Aanloop

1.14.2. Aanloopmethoden



1.14.2.2. Variatie in de ankerweerstand

Opgenomen nominaal vermogen in kW	$k = I_{max}/I_{nom}$
tot 0,25 kW	5
van 0,25 kW tot 0,75 kW	3
van 0,75 kW tot 1,5 kW	2,5
van 1,5 kW tot 10 kW	2
boven 10 kW	1,5

Bron : <http://slptech.be/Cursussen/DCmachines/3%20DC%20motoren%20wm.pdf>

1.15 Remmen

1.15.1. Remweerstand

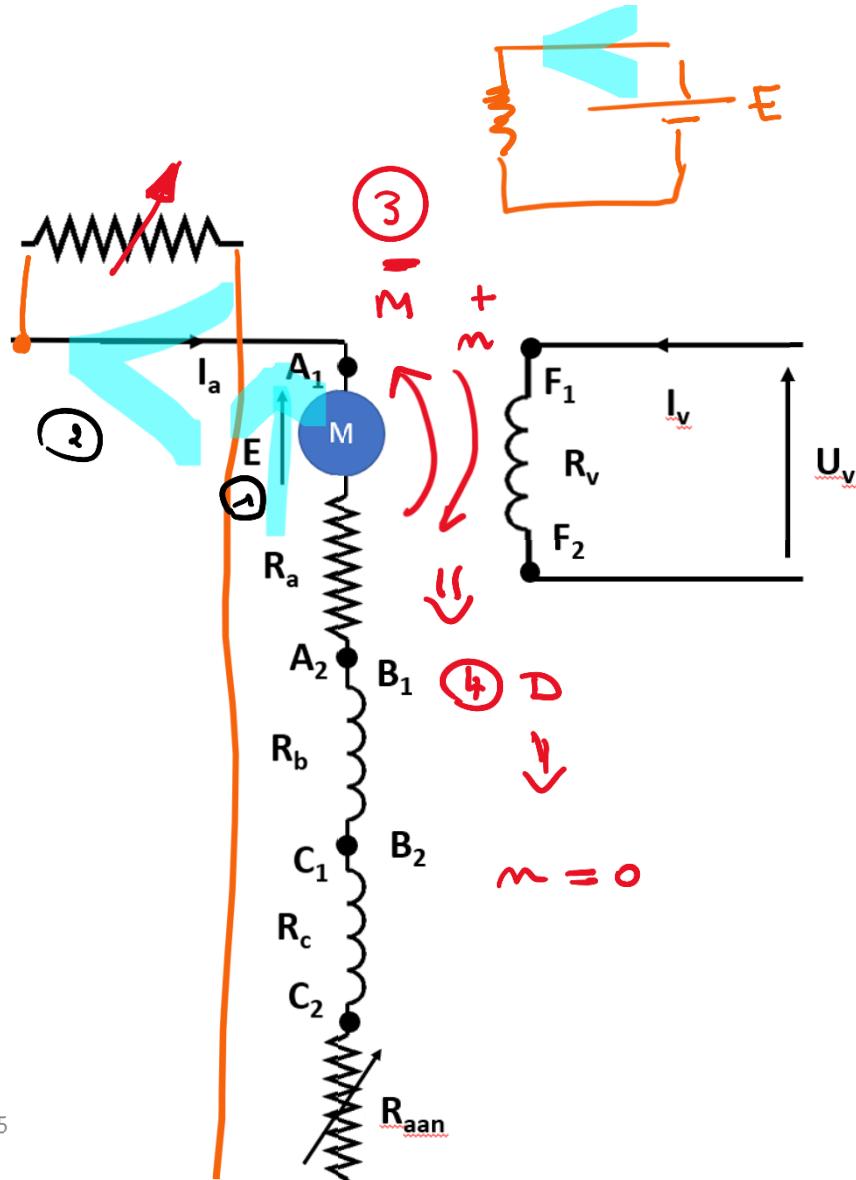
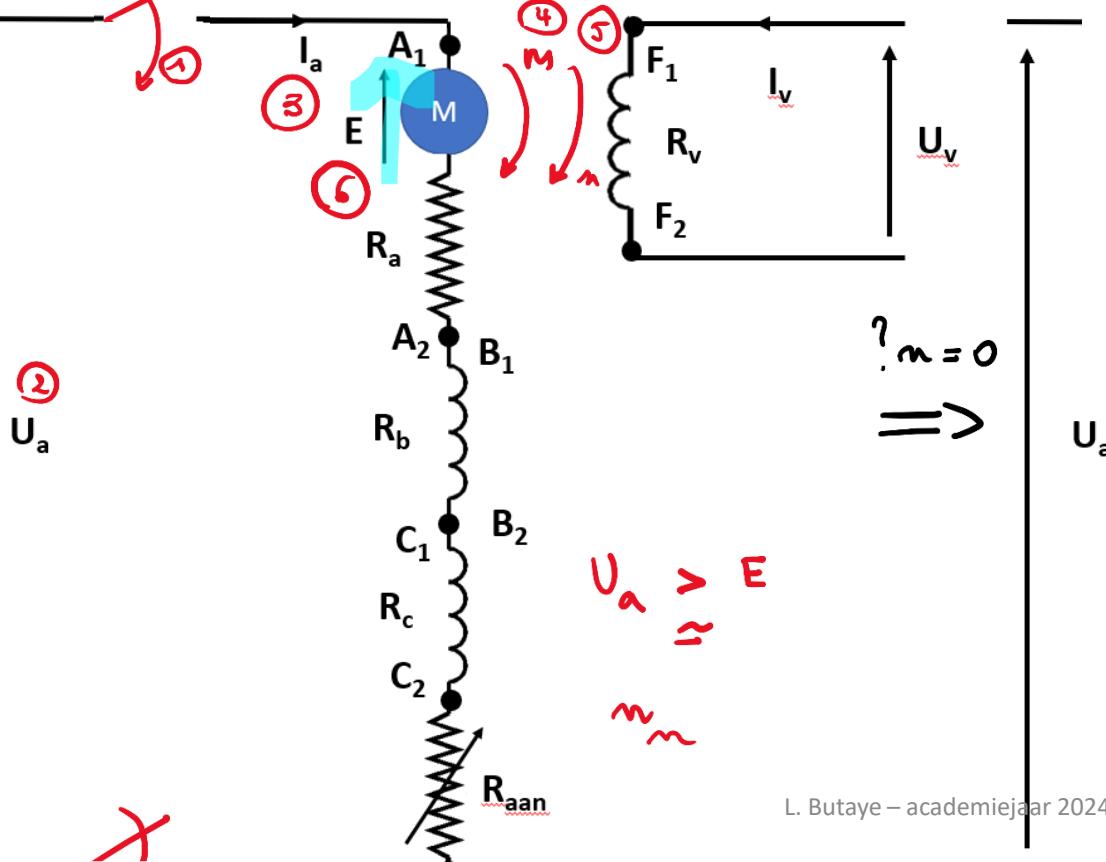


$$\text{---} \rightarrow E \approx U_a$$

$$I_a = \frac{U_a + E}{R_{\text{ator}}}$$

1.15 Remmen

1.15.2. Tegenstroomremmen

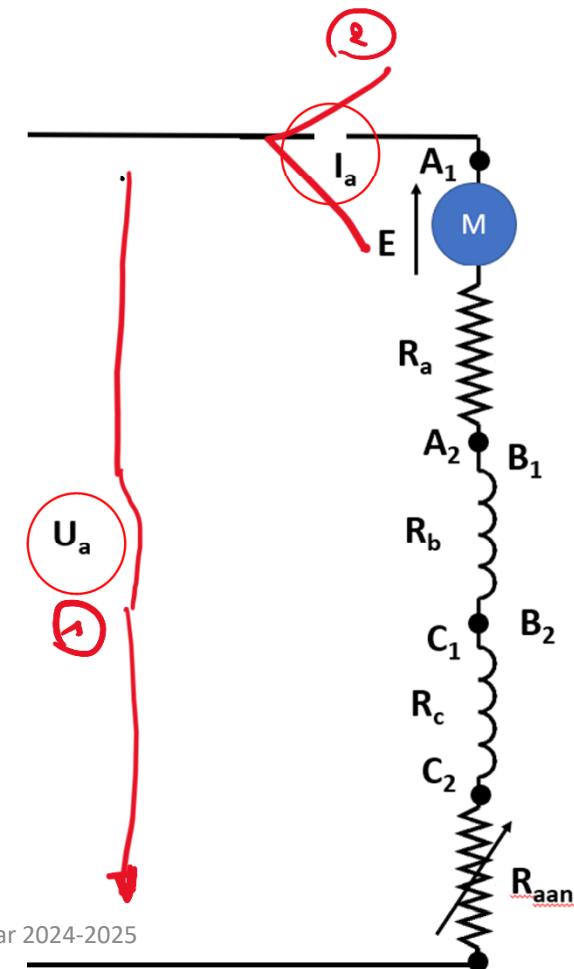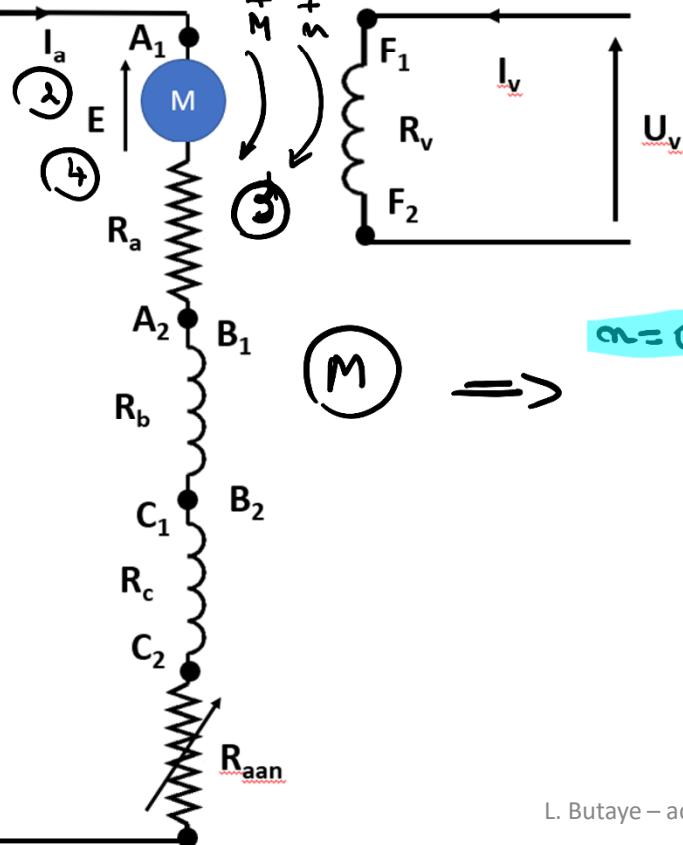

$$\approx \frac{2U_a}{R_{\text{ator}}}$$

\Downarrow
① $I_a \gg$

② m
ongeheerde
zin ??

1.15 Remmen

1.15.3 Recuperatief remmen

